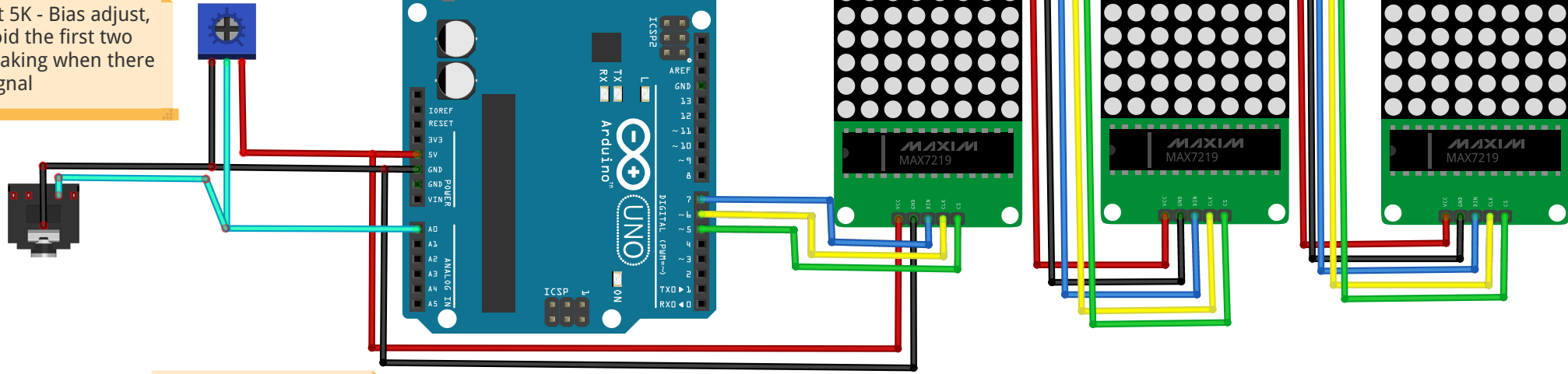


Trimpot 5K - Bias adjust, this avoid the first two bars peaking when there is no signal



If you prefer, use the outputs of an 1 or 2 watt amplifier united together with two 1k resistors in series to get both left and right signals (see the resistos next), use the amp's pot to adjust the signal strength, amps that uses a LM386 with the inverting input to ground, TEA2025B, any wich the ground of the output is common to the ground of the power supply

